
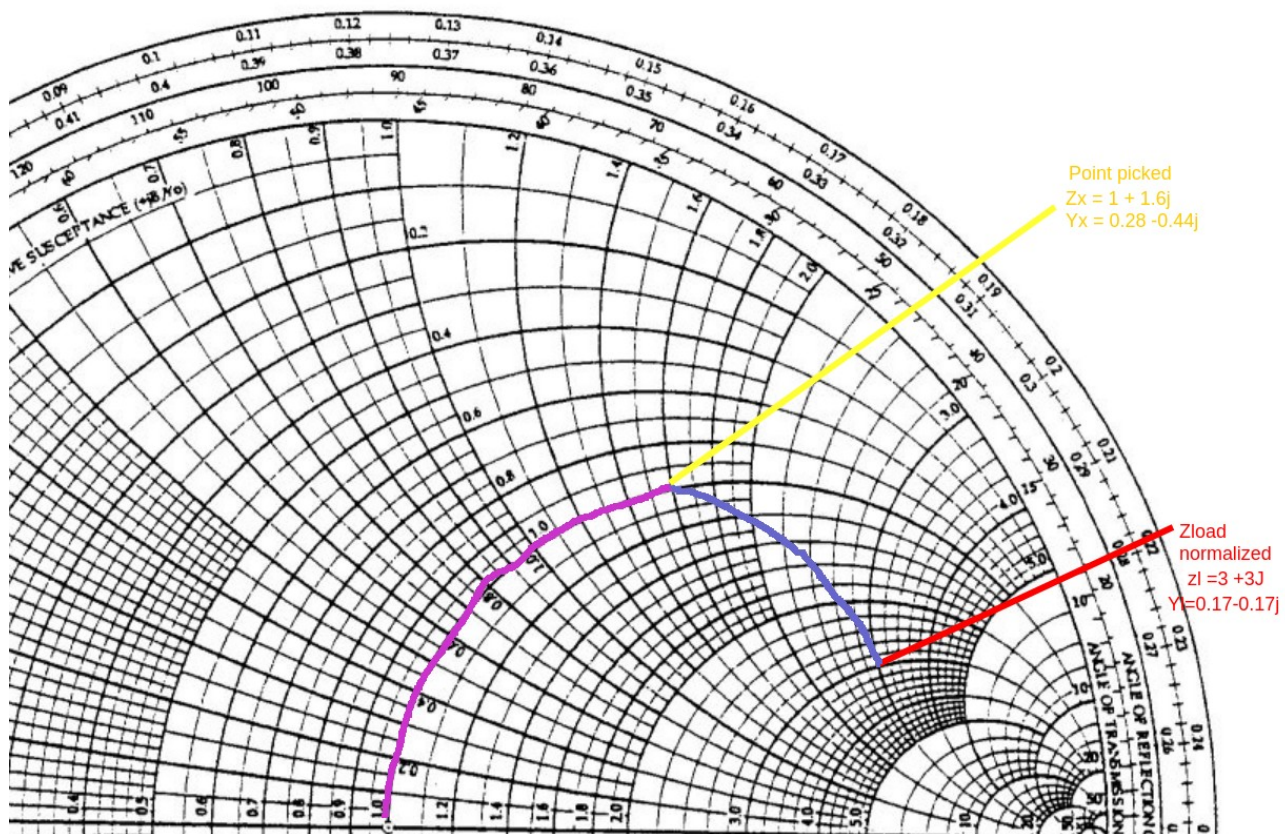


Normalizing Load Impedance Z_L

$$Z_L = (150 + 150j)/50 = 3 + 3j\Omega$$

Normalizing Input impedance

$$Z_{in} = 50/50 = 1\Omega$$

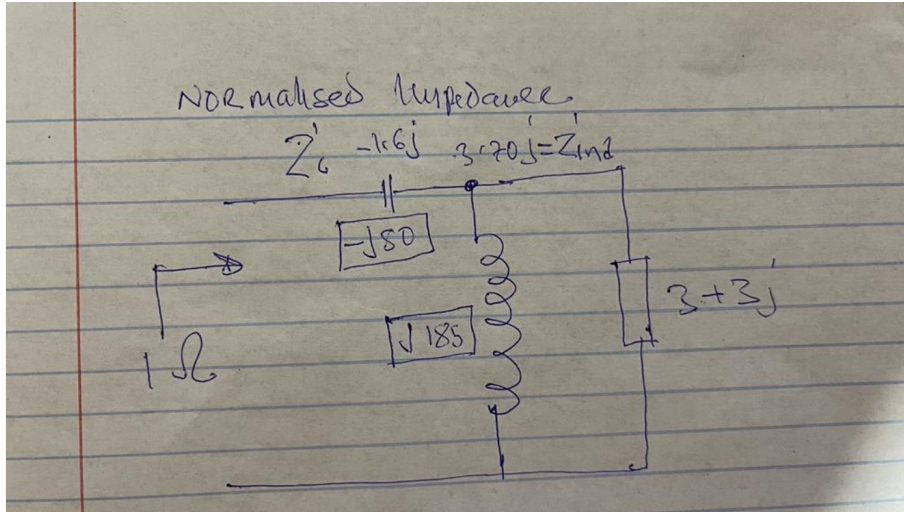

Philip Sisa M. sisaphilip@gmail.com

smith chart sketch

Admittance for Z_1 (Y_1) = $R/(R^2 + X^2) + j(X/(X^2 + R^2))$

$$\begin{aligned} &= 3/(3^2 + 3^2) + j(3/(3^2 + 3^2)) \\ &= 0.166 - j0.166 \dots \dots \dots i \end{aligned}$$

Point selected is at $Z_x = 1 + 1.6j \dots \dots \dots k$

Admittance at this point $Y_x = R/(R^2 + X^2) + j(X/(X^2 + R^2))$

$$\begin{aligned} &= 1/(1 + 1.6^2) + j(1/(1 + 1.6^2)) \\ &= 0.28 - j0.44 \dots \dots \dots ii \end{aligned}$$

Admittance for the $Y_{\text{inductance}}$ is obtained by getting the difference btn Y_1 and Y_x for equation I and ii above

$$\begin{aligned} Y_{\text{ind}} &= -j0.27 \\ Z_{\text{ind}} &= 1/-0.27 = -j3.7 \Omega \end{aligned}$$

Impedance of the capacitor in the Marched network.
From eqn k and 1 ohms

the difference is $-j1.6$ which is equivalent capacitor impedance Z_c

After de-normalizing

$$\begin{aligned} Z_c &= -1.6 * 50 = -j80 \Omega \\ Z_{\text{ind}} &= -3.7 * 50 = -j185 \Omega \end{aligned}$$

Converting inductor into stub line equivalent

reading form the chart for $j3.7$ is equivalent to 0.21λ

